



ELECTRONIC DEVICES

SEMICONDUCTORS:

Solid semiconductors are substances which have their electrical conductivities lying between that of good conductors and insulators.

Intrinsic semiconductor:

Semiconductors without any impurity are called intrinsic semiconductors. For example Germanium (Ge) and silicon (Si).

All temperatures near absolute zero, pure Ge and Si behaves like perfect insulators. But their conductivities increases with increase in temperature. For Germanium, the binding energy of an electron in the covalent bond is 0.7 eV.


In conductors (metals) free electrons act as charge carriers. In insulators there are no free electrons, while on intrinsic semiconductors both electrons and holes act as charge carriers.

When the temperature is increased, the resistance of a conductor increases but the resistance of semiconductor decreases.


a covalent bond with indium. The absence of an electron is called a hole.

Each hole is regarded as a positive charge at that point.

P-N JUNCTION:

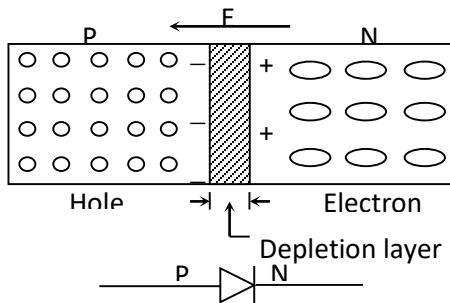


Forward Biasing:

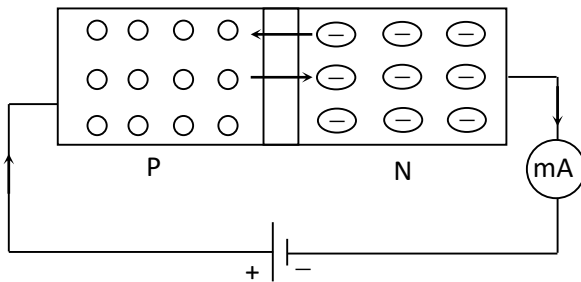


In this case, when the applied p.d. is greater than the barrier p.d. the diode starts conducting. The direction of hole current is same as that of the conventional current.

Reverse Biasing:

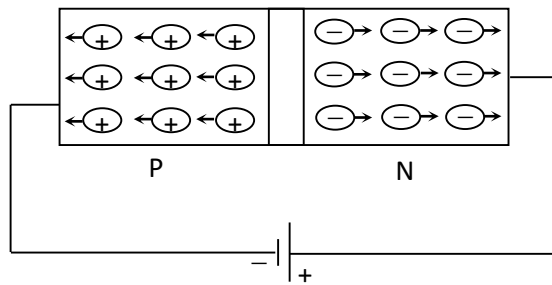


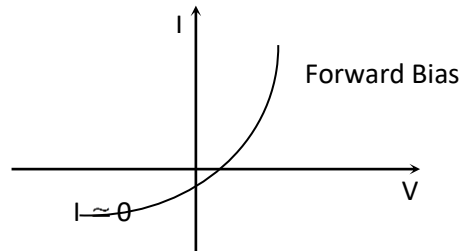
Width of depletion region increased and it acts like an insulator. This current flow due to majority carriers is zero.



P–N JUNCTION DIODE AS RECTIFIER:

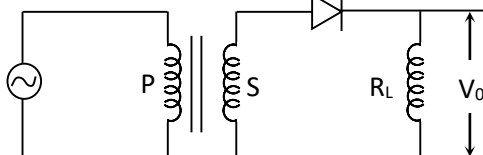(a) P–N junction Diode as Full wave Rectifier:



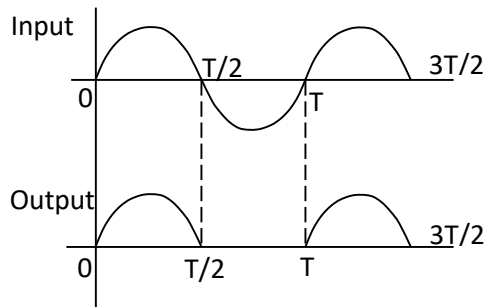



During the positive half cycle of the input voltage the diode is forward biased hence it conducts and current flows through R_L .

In the negative half cycle of the input voltage the diode is reverse biased and hence no current flows through R_L .

Thus V_0 is unidirectional. Hence it is called as half-wave rectifier.

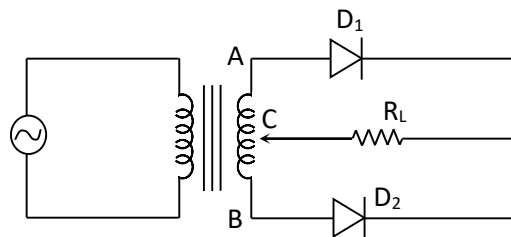(b) P–N junction Diode as Full wave Rectifier:






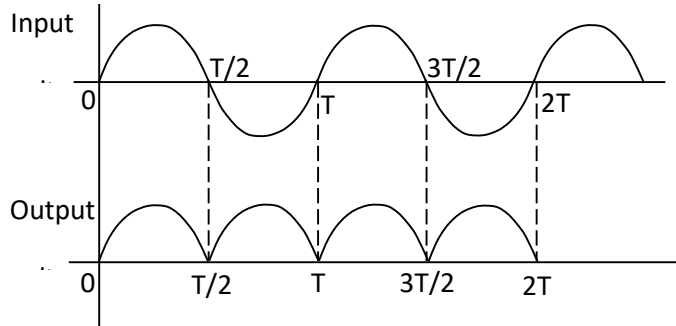


In the positive half cycle, A is positive w.r.t. C and B has an equal negative voltage. In this case D_1 is forward biased hence it conducts but D_2 is reverse biased and it does not conduct.


In the negative half cycle of input voltage; B is positive w.r.t. C and A has an equal negative voltage. In this case D_2 is forward biased hence it becomes conducting and D_1 becomes non-conducting.

Since the current flows through R_L in both halves of the input cycle and since the AC input voltage is falling converted into DC voltage, the arrange is called a full wave rectifier.

TRANSISTOR:

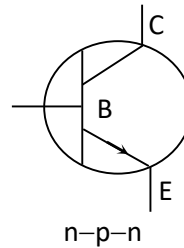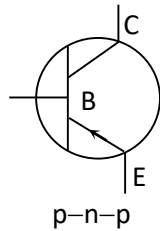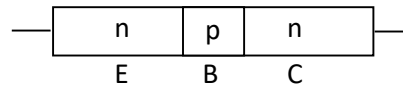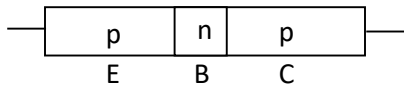

Action in Transistor:

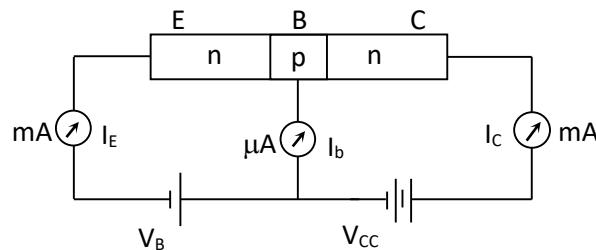

The emitter base junction is forward biased. Some of the electrons combine with the hole in the base and constitute the base current I_b . The electron current flowing from emitter to base forms the emitter current I_E .


The collector base junction is reverse biased. Hence the electrons are attracted towards the collector, which is maintained

at a higher positive potential. The motion of these electrons gives rise to the collector current I_C .

According to Kirchoff's law

$$I_E = I_C + I_B$$

Amplifying action of a Transistor:

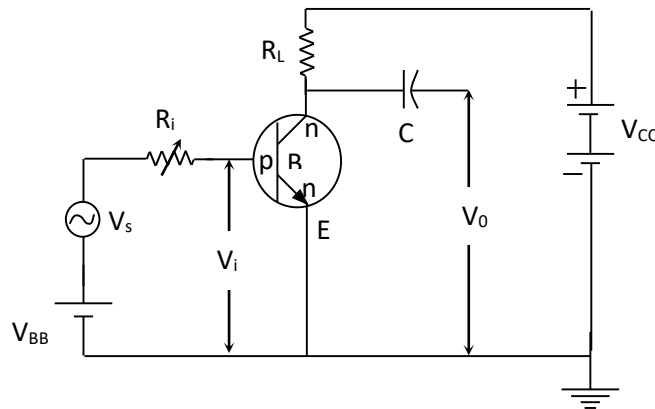

In common current emitter transistor amplifier,

β_{dc} = DC current gain = $\frac{I_C}{I_B}$ when any input signal is not applied

β_{ac} = AC current gain = $\frac{\Delta I_C}{\Delta I_B}$ when V_s is supplied.

Similarly, voltage gain = $\frac{R_L \Delta I_C}{R_i \Delta I_B} = \beta \frac{R_L}{R_i}$



So, power gain = voltage gain \times current gain

$$= \beta \frac{R_L}{R_i} \times (\beta) = \beta^2 \frac{R_L}{R_i}$$

In common Base transistor amplifier,

$$\text{DC current gain } \alpha = \frac{I_C}{I_E}$$

$$\text{AC current gain } \alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

$$\text{AC voltage gain} = \frac{\Delta V_C}{\Delta V_i} = \frac{\Delta I_C R_L}{\Delta I_E R_i}$$

$$= \alpha_{ac} \times \frac{R_o}{R_i}$$

Where $\frac{R_o}{R_i}$ is called resistance gain

$$\text{AC power gain} = \frac{\Delta V_C \times \Delta I_C}{\Delta V_i \Delta I_E} = \alpha_{ac} \times \frac{R_o}{R_i} \alpha_{ac} = \alpha_{ac}^2 \times \frac{R_o}{R_i}$$

Logic gates:

A digital circuit with one or more input signals but only one output signal is known as logic gate. There are three basic logic gates:

- (i) OR gate (ii) AND Gate (III) NOT Gate


OR gate

The functional statement for 'OR' gate is the output (Y) of 'OR' gate will be 1 when the input A or B or both are 1.

The OR gate in terms of Boolean expression is

$$A + B = Y$$

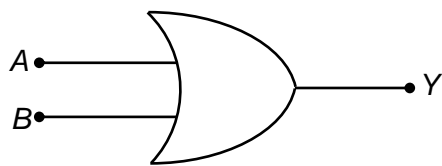This statement can also be given in the form of a table known as truth table, which is given below



Truth table of two input OR gate.


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

AND GATE

The functional statement for AND gate is the output Y of AND gate is 1, if all the inputs simultaneously have the state 1. The AND gate in terms of Boolean expression is

$$Y = A.B$$

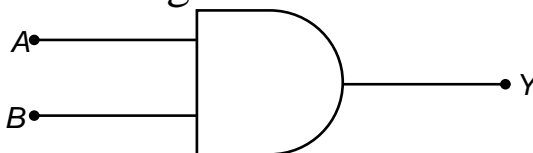
The above function can be stated in the form of the following truth table



Truth table of AND gate

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

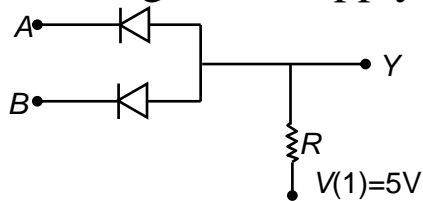
There is no supply current and hence no drop across R only when both A and B are at $+5V$. Only in that case the output Y goes to supply a voltage of $+5V$.



NOT GATE

The output of the NOT gate is not same as the input, we can say that it performs a negation operation on the input.

The truth table is given below

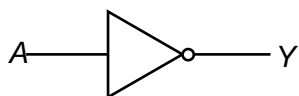

Truth table of NOT gate


A	Y
0	1
1	0

NOR GATE

If we put an NOT Gate at the output of OR Gate gives a NOT of OR gate or NOR gate. The Boolean equation for



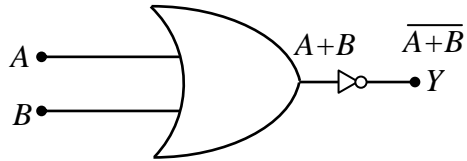NOR gate is $Y = \overline{A+B}$. Truth table for NOR gate can be written as follows.



The NOR Truth Table

A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate is a universal gate because we can obtain all the possible gates by using this NOR gate as basic building block.