
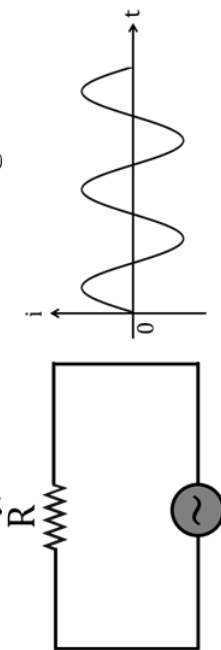


Alternating Current

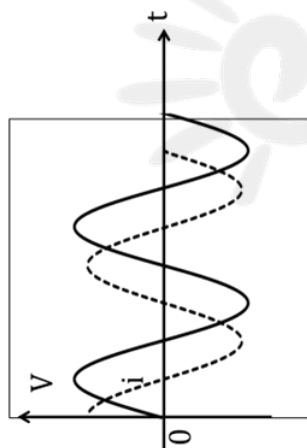If the direction of current changes alternately, it is called Alternating Current.



$$V = V_0 \sin(\omega t)$$



Average Value of a Function

$$\langle y \rangle = \frac{\int y dt}{\int dt}$$

Average value of y

- (i) $\langle \sin(\omega t + \phi) \rangle = 0$
- (ii) $\langle \cos(\omega t + \phi) \rangle = 0$
- (iii) $\langle \sin^2(\omega t + \phi) \rangle = \frac{1}{2}$
- (iv) $\langle \cos^2(\omega t + \phi) \rangle = \frac{1}{2}$

MIND MAP

Alternating current

RMS (Root Mean Square) Value of a Function

$$y_{\text{rms}} = \sqrt{\langle y^2 \rangle}$$

$$\text{Where } \langle y^2 \rangle = \frac{\int y^2 dt}{\int dt}$$

- (i) $\langle \sin(\omega t + \phi) \rangle_{\text{rms}} = \frac{1}{\sqrt{2}}$
- (ii) $\langle \cos(\omega t + \phi) \rangle_{\text{rms}} = \frac{1}{\sqrt{2}}$

Pure Resistive Circuit



$$V = iR$$

$$i = \frac{V}{R} = \frac{V_0 \sin(\omega t)}{R}$$

$$i = i_0 \sin(\omega t)$$

$$i_0 = \frac{V_0}{R} \quad i_{\text{rms}} = \frac{V_{\text{rms}}}{R}$$

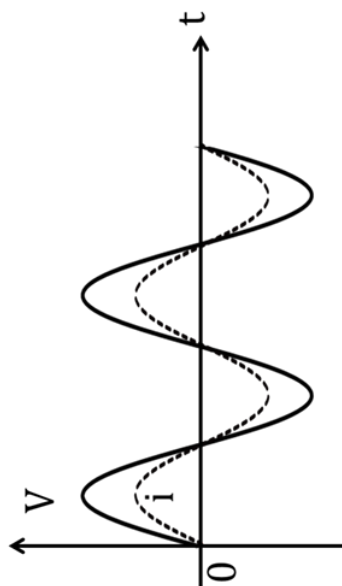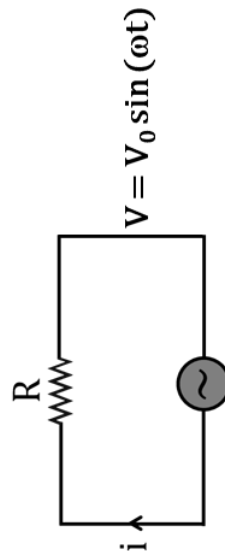
$$i_{\text{rms}} = \frac{i_0}{\sqrt{2}} \quad V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$



Keypoint

$$V = V_0 \sin(\omega t) \quad i = i_0 \sin(\omega t)$$

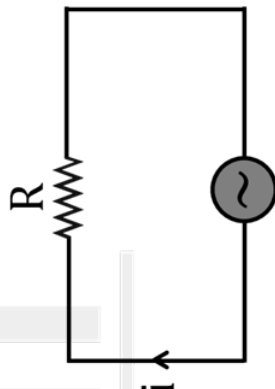
In pure resistive circuit V and i are in same phase.



$$V = V_0 \sin(\omega t)$$

- 220V is the rms value of Voltage in India.
- $f = 50\text{Hz}$
- $\omega = 2\pi f = 100\pi$

Pure Capacitive Circuit

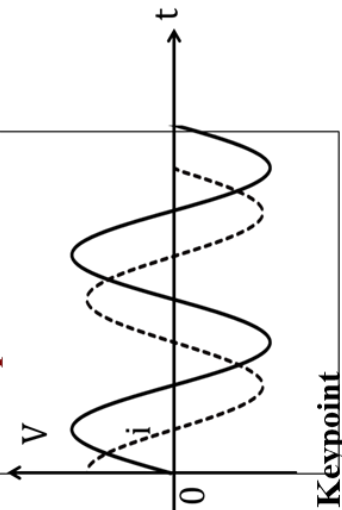


Keypoint

$$V = V_0 \sin(\omega t) \quad i = i_0 \sin\left(\omega t + \frac{\pi}{2}\right)$$


In pure Capacitive circuit Current leads

Voltage by phase $\frac{\pi}{2}$

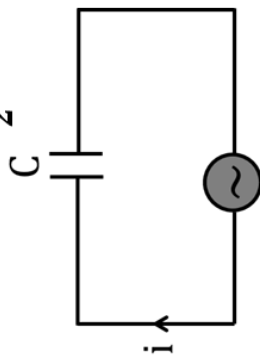

$$V = V_0 \sin(\omega t)$$

Pure Inductive Circuit

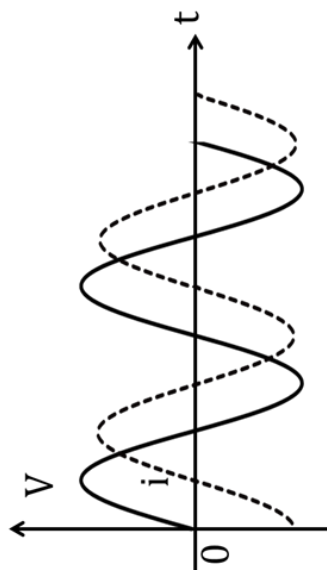

MIND MAP


Alternating current

Keypoint

$$V = V_0 \sin(\omega t) \quad i = i_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

In pure Inductive circuit Voltage leads

Current by phase $\frac{\pi}{2}$

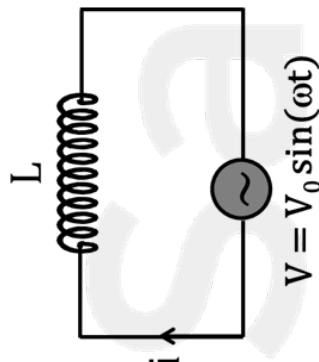


$$V = V_0 \sin(\omega t)$$

Impedance

$$i_0 = \frac{V_0}{R}$$


$$i_0 = \frac{V_0}{X_C}$$

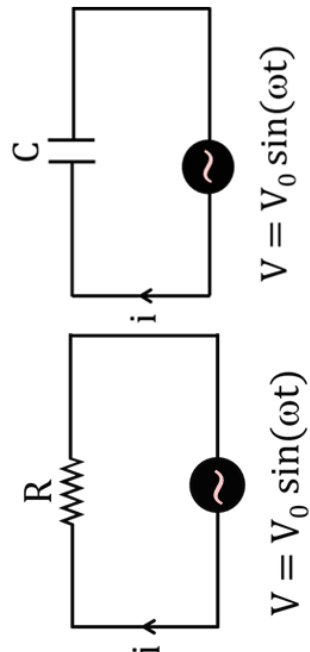

$$V = V_0 \sin(\omega t)$$

$$V = V_0 \sin(\omega t)$$

$$i_0 = \frac{V_0}{X_L}$$

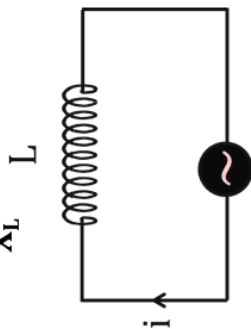


$$i_0 = \frac{V_0}{Z}$$

Impedance


$$V = V_0 \sin(\omega t)$$

L-C-R Circuit

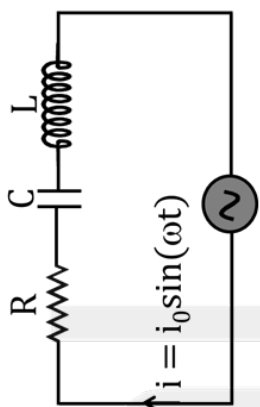

$$V = V_0 \sin(\omega t + \phi)$$

$$V_{L_0} - V_{C_0}$$

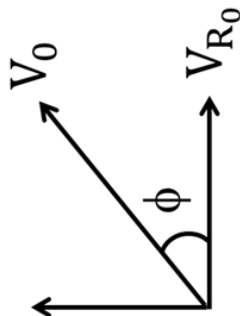


$$i_0 = \frac{V_0}{Z} \quad i_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2} \quad \tan \phi = \frac{X_L - X_C}{R}$$

MIND MAP

Alternating current

Resonance in LCR Circuit

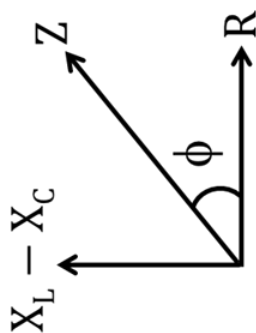

If $X_L > X_C$ circuit is predominantly Inductive (V leads i)

If $X_L < X_C$ circuit is predominantly Capacitive (i leads V)

Power Factor

$$\langle P \rangle = i_{\text{rms}} V_{\text{rms}} \cos \phi$$


$$\cos \phi = \frac{R}{Z}$$

Energy loss in pure capacitance in AC circuit is zero

Power dissipated in pure inductance in AC circuit is zero

Power Factor of L-R circuit is
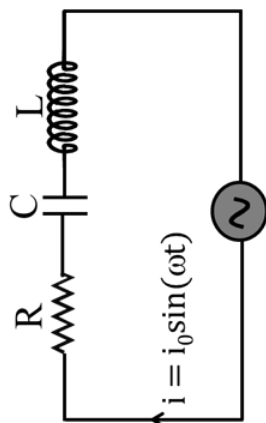
$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + X_L^2}}$$



$$V = V_0 \sin(\omega t + \phi)$$

$$i_0 = \frac{V_0}{Z} = \frac{V_0}{\sqrt{(X_L - X_C)^2 + R^2}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

i_0 will be maximum when $X_L = X_C$

$$\Rightarrow \omega L = \frac{1}{\omega C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$


$$i_0 = \frac{V_0}{\sqrt{(X_L - X_C)^2 + R^2}} = \frac{V_0}{\sqrt{\left(\omega L - \frac{1}{\omega C}\right)^2 + R^2}}$$

At Resonance

(1) i_0 will be maximum (2) $X_L = X_C$

(3) $Z=R$ (4) $\cos \phi=1$

(5) $\omega_0 = \frac{1}{\sqrt{LC}}$

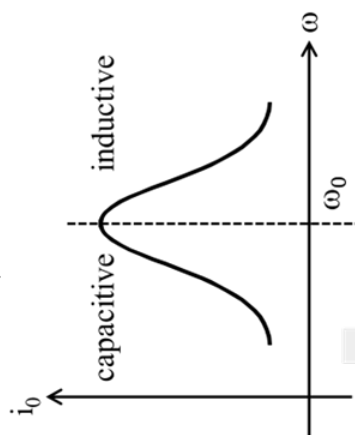


Transformers

Transformer is used to change (i.e. transform) an alternating voltage from one value to another using principle of mutual induction.



$$V_p = -N_p \frac{d\phi}{dt} \quad V_s = -N_s \frac{d\phi}{dt}$$

$$P = vi$$

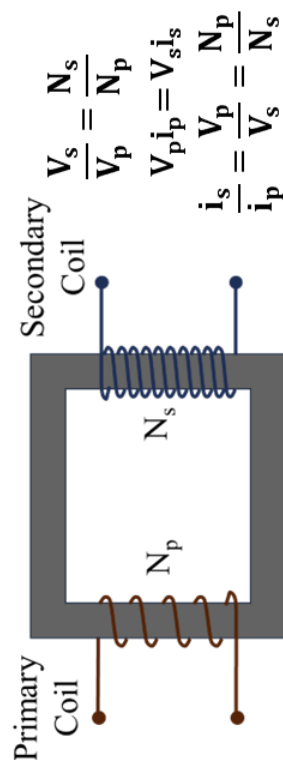


MIND MAP

Alternating current

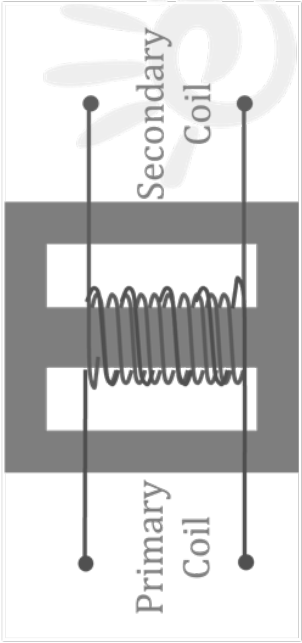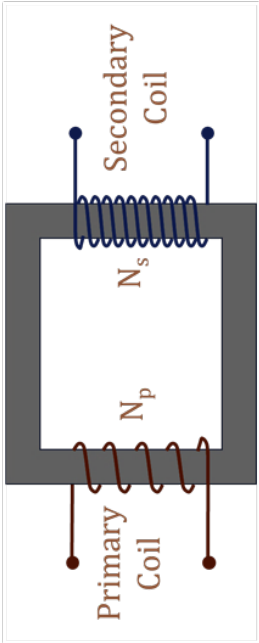

LC Oscillations

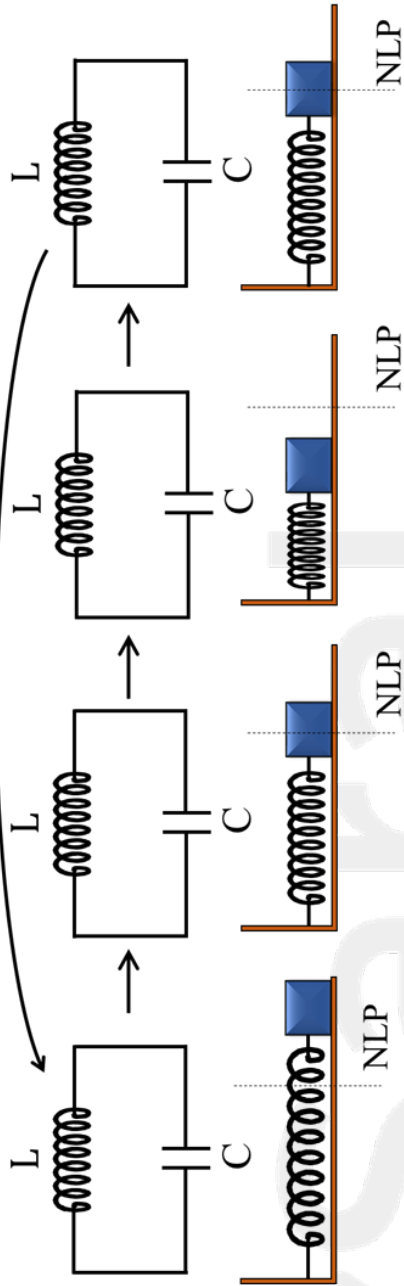


Cause	Rectification	Cause	Rectification
(1) Flux Leakage: Due to poor design and air gaps in the core, all the flux due to primary does not pass through the secondary.	(1) By winding the primary and secondary coil one over the other.	(3) Eddy Currents: The alternating magnetic flux induces eddy currents in the core and causes heating.	(3) By using laminated core it can be reduced.
(2) Resistance of the windings: causes heat loss.	(2) In high current, low voltage windings, these are minimized by using thick wire.	(4) Hysteresis: Alternating magnetization of core cause hysteresis loss.	(4) It is kept minimum by using a magnetic material having low hysteresis loss.

LC & Spring Block

MIND MAP

Alternating current

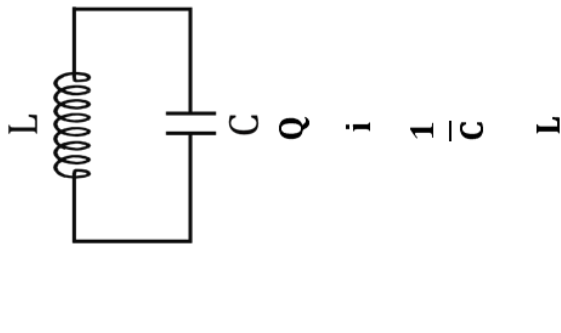


Electrical energy $\frac{Q^2}{2C}$
Magnetic energy $\frac{1}{2}Li^2$

$$\frac{Q_0^2}{2C} = \frac{1}{2}Li_0^2 = \frac{Q^2}{2C} + \frac{1}{2}Li^2$$




Potential energy $\frac{1}{2}kx^2$
Kinetic energy $\frac{1}{2}mv^2$
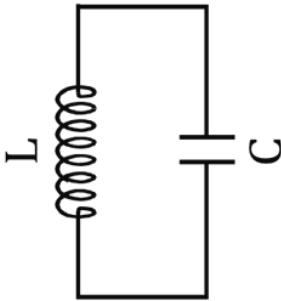
$$\frac{1}{2}RA^2 = \frac{1}{2}mv_{\text{man}}^2 = \frac{1}{2}kn^2\frac{\pi}{2}m_v^2$$



$$i = \omega \sqrt{Q_0^2 - Q^2}$$
$$i_{\text{max}} = \omega Q_0$$
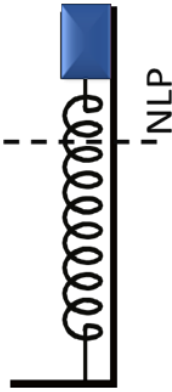
$$\omega = \frac{1}{\sqrt{LC}} \quad ; \quad T = 2\pi\sqrt{LC}$$



$$v = \omega \sqrt{A^2 - x^2}$$

$$V_{\text{max}} = \omega A$$

$$\omega = \sqrt{\frac{k}{m}} \quad ; \quad T = 2\pi\sqrt{\frac{m}{k}}$$