

Capacity of a Capacitor depends on

- 1) Shape and size of the plates
- 2) Distance between plates
- 3) Medium between the plates


Parallel Plate Capacitor $C = \frac{A\epsilon_0}{d}$

Spherical Capacitor

$$C = \frac{4\pi\epsilon_0 ab}{b-a}$$

Cylindrical Capacitor
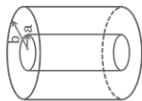
$$C = \frac{2\pi\epsilon_0 l}{\ln\left(\frac{b}{a}\right)}$$



Series Combination (charge is same), $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

Parallel Combination (V is same), $C_{eq} = C_1 + C_2 + \dots$

Mesh Analysis

- Assume charge using Junction Law.

- Apply KVL

Nodal Analysis

- Assume potential in a circuit.
- Apply Junction Law

Work Done By Battery

$$W = QV$$

Energy Stored in a Capacitor $= \frac{1}{2} CV^2 = \frac{Q^2}{2C} = \frac{1}{2} QV$

Electrostatic Force b/w the Plates of a Parallel Plate Capacitor

$$F = \frac{Q^2}{2A\epsilon_0}$$

MIND MAP

Capacitor

Bound Charges (Induced Charges) on Dielectric $q = Q \left(1 - \frac{1}{K}\right)$

Heat Loss $= \frac{Q_0^2}{2C}$

Capacity of a Capacitor, $C = \frac{Q}{V}$. Battery is not connected


where C is a +ve constant for a conductor and is called capacity (capacitance) of capacitor.

SI unit of Capacity is Farad

Before	After
Q_0	Q_0
C_0	KC_0
E_0	E_0/K
V_0	V_0/K
U_0	U_0/K

Before	After
Q_0	KQ_0
C_0	KC_0
E_0	E_0
V_0	V_0
U_0	$U_0 K$

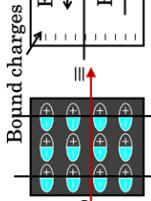Dielectric
Polar (Eg. H_2O) have dipoles even in absence of external $\vec{E}$
Non-Polar (Eg. Graphite) do not have dipoles in absence of external $\vec{E}$



$$E_{net} = E_0 - E_{int}$$

$$E_{net} = \frac{E_0}{K} \quad [K \text{ is dielectric constant}]$$

Vacuum $1 \leq K \leq \infty$
Conductors

Dielectric Inside Capacitor $E_{net} = \frac{E_0}{K}$ $C = KC_0$

Effect on Parameters due to Introduction of Dielectric Slab (Completely Filled)

2. Battery is connected

Before	After
Q_0	KQ_0
C_0	KC_0
E_0	E_0
V_0	V_0
U_0	$U_0 K$

Conductor Capacitor

$Q \rightarrow$ Charge on conductor $Q \rightarrow$ Charge on positive plate

$V \rightarrow$ Potential of conductor $V \rightarrow$ Potential difference between plates


1 Farad is a very BIG unit. $\mu F(10^{-6}F), nF(10^{-9}F), pF(10^{-12}F)$

Heat Generated in Circuit $H = \sum W_b - \sum \Delta E$

$$\Delta E = (E_f - E_i)$$

$$\sum W_b = \text{Work done by all batteries}$$
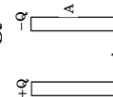
$$\sum \Delta E = \text{Energy change in all capacitors}$$



Charging of Capacitor


$$q = CE(1 - e^{-t/RC})$$

$$i = \frac{E}{R}(e^{-t/RC})$$


Time Constant (τ) $\tau = RC$

After 1τ time capacitor gets 63% charged

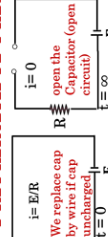Calculation of current at $t = 0$ and $t = \infty$



Discharging of Capacitor

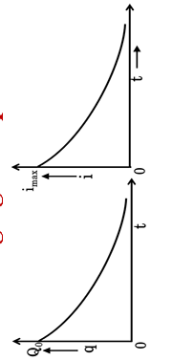

In 1τ approx capacitor $q = Q_0 e^{-t/RC}$
63% discharged $i = i_{max} e^{-t/RC}$